



컴퓨터공학 기초 실험2


Lab #4

Carry Look-ahead Adder(CLA)


CARRY LOOK-AHEAD ADDER

Carry Look-ahead Adder

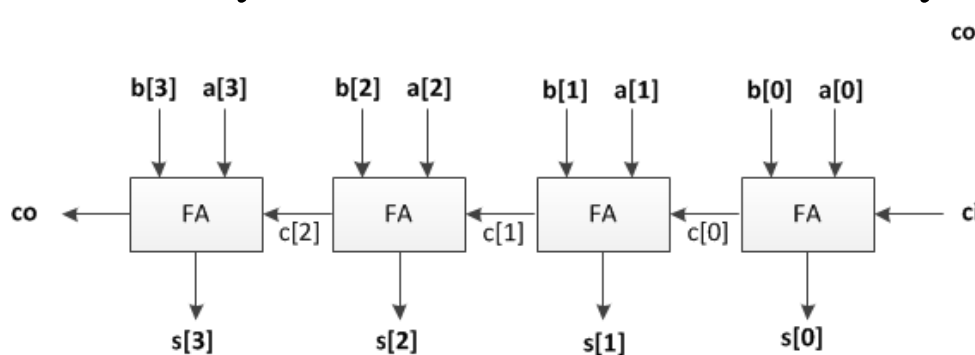- Ripple Carry Adder(RCA)가 계산이 완료될 때까지의 시간이 많이 걸리는 단점을 보완하기 위해 입력 a , b 그리고 carry가 주어질 때, 모든 올림수가 동시에 구해져 계산시간을 단축시킨 가산기
 - ✓ Carry만을 계산해주는 별도의 carry look-ahead block이 존재



RCA

 

CLA

Carry Look-ahead Adder(Cont.)

- CLA로 carry out 값을 미리 계산해주기 위해서는 generation signal(G_i), propagation signal(P_i)을 아래와 같이 정의한다.

$$G_i = A_i B_i$$

$$P_i = A_i + B_i$$

- 위 식을 full adder의 carry out에 적용하면 다음과 같다.

$$C_{i+1} = A_i B_i + (A_i + B_i) C_i = G_i + P_i C_i$$

- 이를 적용하여 4-bit adder의 carry를 미리 계산하면 다음과 같다.

$$\begin{aligned} C_1 &= \\ C_2 &= \\ C_3 &= \\ C_{out} &= \end{aligned}$$

Boolean Equation

4-bit Carry Look-ahead Adder

PRACTICE I


Carry Look-ahead Adder

➤ New Project Wizard

- ✓ Project name : cla4
- ✓ Family & Device : Cyclone V 5CSXFC6D6F31C6 (밑에서 6번째)

➤ Verilog file

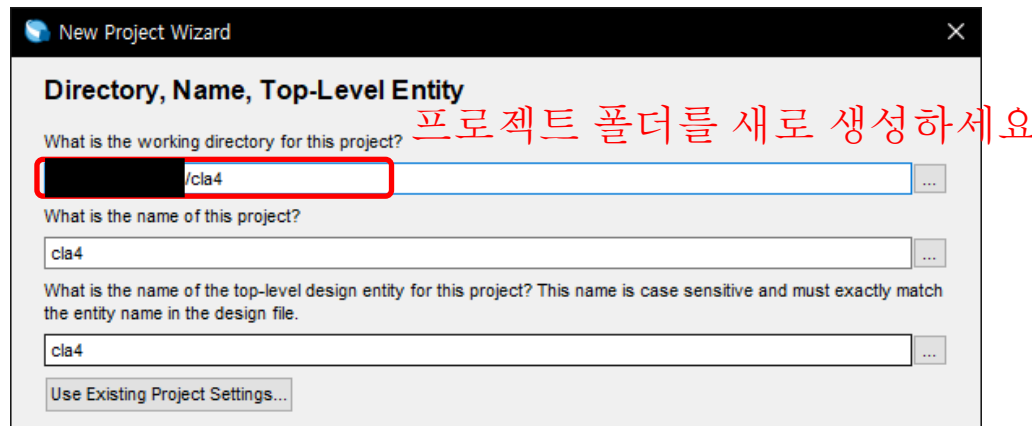- ✓ Add file : gates.v
- ✓ New file : fa_v2.v, clb4.v, cla4.v, tb_cla4.v



Basic Logic Gates (1/2)

➤ Inverter

```
module _inv(a,y);  
input a;  
output y;  
assign y=~a;  
endmodule
```

➤ 2-to-1 nand gate

```
module _nand2(a,b,y);  
input a,b;  
output y;  
assign y=~(a&b);  
endmodule
```

➤ 2-to-1 and gate

```
module _and2(a,b,y);  
input a,b;  
output y;  
assign y=a&b;  
endmodule
```

➤ 2-to-1 or gate

```
module _or2(a,b,y);  
input a,b;  
output y;  
assign y=a|b;  
endmodule
```

➤ 2-to-1 xor gate

```
module _xor2(a,b,y);  
input a, b;  
output y;  
wire inv_a, inv_b;  
wire w0, w1;  
_inv U0_inv(.a(a), .y(inv_a));  
_inv U1_inv(.a(b), .y(inv_b));  
_and2 U2_and2(.a(inv_a), .b(b), .y(w0));  
_and2 U3_and2(.a(a), .b(inv_b), .y(w1));  
_or2 U4_or2(.a(w0), .b(w1), .y(y));  
endmodule
```

Basic Logic Gates (2/2)

➤ 3-to-1 and gate

```
module _and3(a,b,c,y);  
input a,b,c;  
output y;  
assign y=a&b&c;  
endmodule
```

➤ 4-to-1 and gate

```
module _and4(a,b,c,d,y);  
input a,b,c,d;  
output y;  
assign y=a&b&c&d;  
endmodule
```

➤ 5-to-1 and gate

```
module _and5(a,b,c,d,e,y);  
input a,b,c,d,e;  
output y;  
assign y=a&b&c&d&e;  
endmodule
```

➤ 3-to-1 or gate

```
module _or3(a,b,c,y);  
input a,b,c;  
output y;  
assign y=a|b|c;  
endmodule
```

➤ 4-to-1 or gate

```
module _or4(a,b,c,d,y);  
input a,b,c,d;  
output y;  
assign y=a|b|c|d;  
endmodule
```

➤ 5-to-1 or gate

```
module _or5(a,b,c,d,e,y);  
input a,b,c,d,e;  
output y;  
assign y=a|b|c|d|e;  
endmodule
```

(Lab 3에 작성한 gates.v에 추가)

Revision of Full Adder

➤ Full Adder

- ✓ RCA에서 작성했던 full adder와 다르게 CLA에서는 full adder의 carry out이 필요하지 않다.
- ✓ module name : fa_v2
- ✓ Exclusive or gate 2개를 instance하여 작성한다.

Input			Output
Ci	a	b	s
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

```
module fa_v2(a,b,ci,s);  
input a,b,ci;  
output s;  
wire w0;
```

Instances

```
endmodule
```

Carry Look-ahead Block (1/2)

➤ Module name : clb4

$G_i =$

$P_i =$

$C_1 =$

$C_2 =$

$C_3 =$

$C_o =$

Boolean Equation

```
module clb4(a,b,ci,c1,c2,c3,co);  
  input [3:0]a,b;  
  input ci;  
  output c1,c2,c3,co;  
  wire [3:0] g,p;  
  wire w0_c1;  
  wire w0_c2, w1_c2;  
  wire w0_c3, w1_c3, w2_c3;  
  wire w0_co, w1_co, w2_co, w3_co;
```

// Generate

Instances about generate signal (Gi)

// Propagate

Instances about propagate signal (Pi)

Carry Look-ahead Block (2/2)

```
// c1 = g[0] | (p[0] & ci);
```

Instances about c1

```
// c2 = g[1] | (p[1] & g[0]) | (p[1] & p[0] & ci);
```

Instances about c2

```
// c3 = g[2] | (p[2] & g[1]) | (p[2] & p[1] & g[0]) | (p[2] & p[1] & p[0] & ci);
```

Instances about c3


```
// co = g[3]  
// | (p[3] & g[2])  
// | (p[3] & p[2] & g[1])  
// | (p[3] & p[2] & p[1] & g[0])  
// | (p[3] & p[2] & p[1] & p[0] & ci)
```

Instances about co

```
endmodule
```

Carry Look-ahead Adder

➤ cla4

 

```
module cla4(a, b, ci, s, co);  
  input [3:0] a, b;  
  input ci;  
  output [3:0] s;  
  output co;  
  
  wire [3:0] c;  
  
  fa_v2 U0_fa  
  fa_v2 U1_fa  
  fa_v2 U2_fa  
  fa_v2 U3_fa  
  clb4 U4_clb4  
endmodule
```

Instances of fa_v2 and clb4

Testbench

➤ Testbench

✓ Functional simulation을 수행

```
`timescale 1ns/100ps


module tb_cla4;
    reg [3:0] tb_a, tb_b;
    reg tb_ci;
    wire [3:0] tb_s;
    wire tb_co;
    wire [4:0] tb_result;

    assign tb_result = {tb_co, tb_s};


    cla4 U0_cla4(.a(tb_a), .b(tb_b), .ci(tb_ci), .s(tb_s), .co(tb_co));

    initial
    begin
        Testbench
    end
endmodule
```

RTL Viewer (1/2)

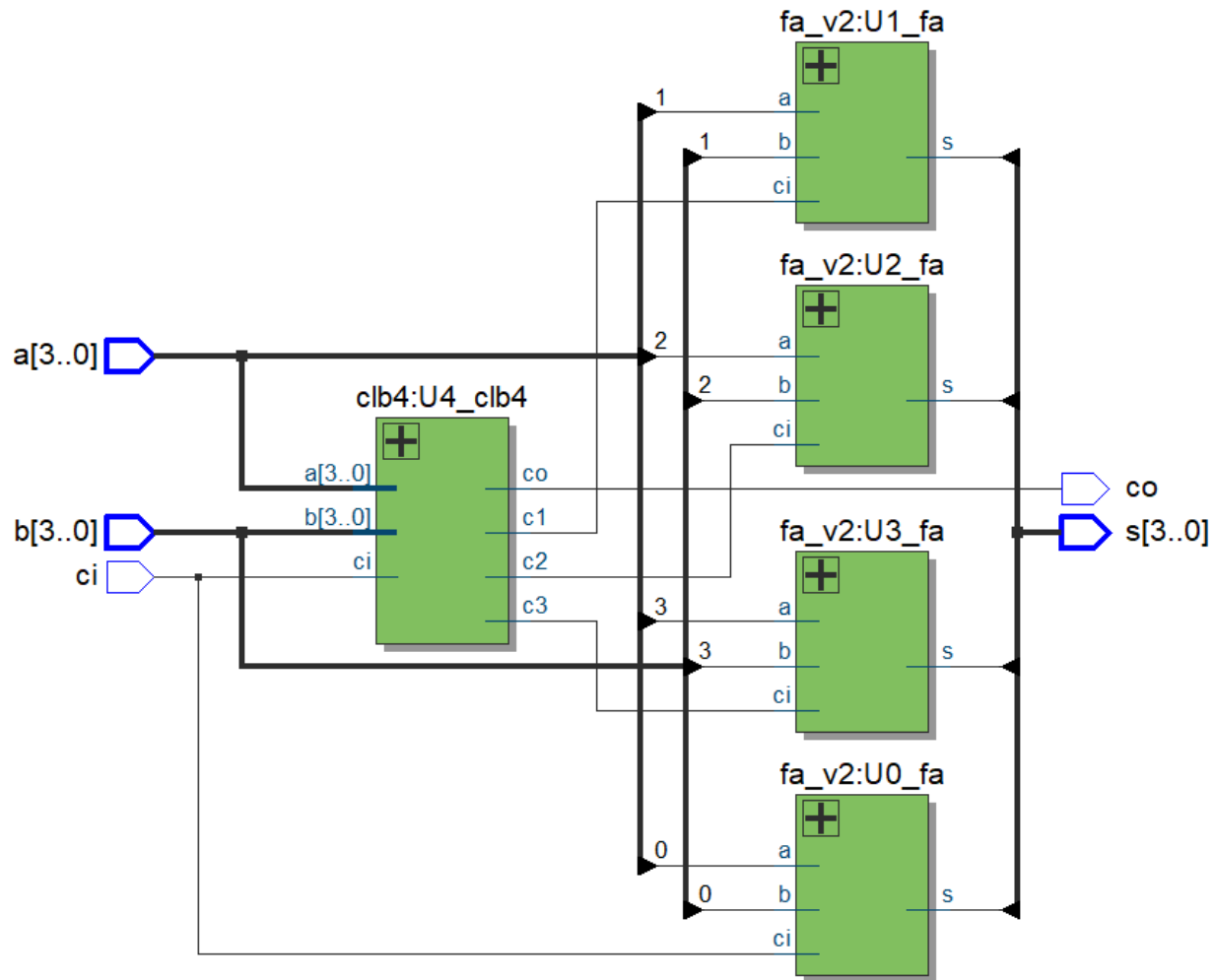

RTL Viewer (2/2)

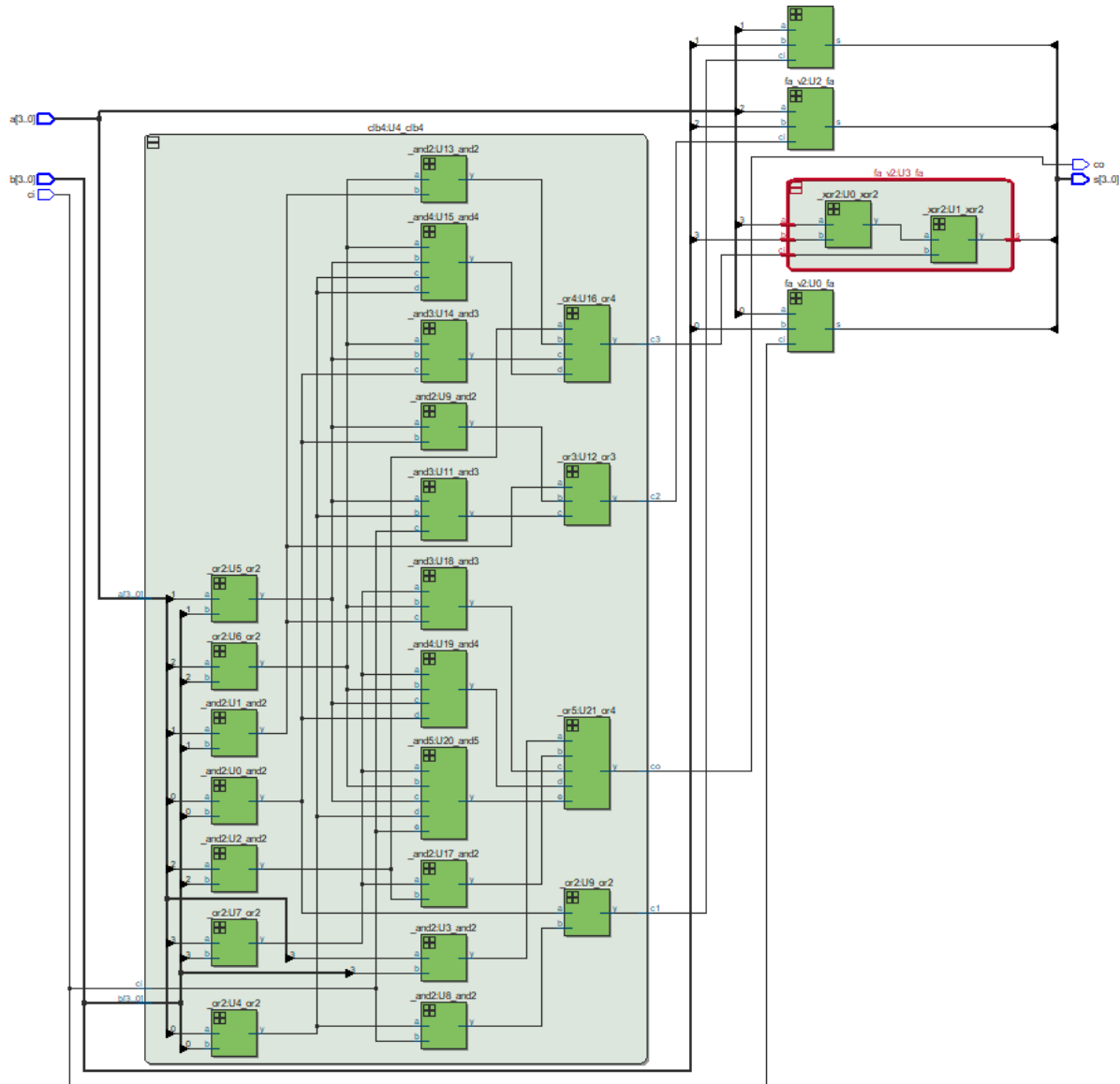

Compilation Report

➤ RCA와 비교하여 본다.

Flow Status	Successful [REDACTED]
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite Edition
Revision Name	[REDACTED]
Top-level Entity Name	cla4
Family	Cyclone V
Device	5CSXFC6D6F31C6
Timing Models	Final
Logic utilization (in ALMs)	N/A
Total registers	0
Total pins	14
Total virtual pins	0
Total block memory bits	0
Total DSP Blocks	0
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0
Total DLLs	0


Timing Analysis of 32-bit CLA

PRACTICE II

Timing Analysis

➤ Timing analysis

 - ✓ **A process of analyzing delays** in a logic circuit to determine the conditions under which the circuit operates reliably
- ✓ These conditions include, but are not limited to, the maximum clock frequency(f_{max}) for which the circuit will produce a correct output



Timing Analysis of CLA

➤ New Project Wizard

- ✓ Project name : cla_clk
- ✓ Family & Device : Cyclone V 5CSXFC6D6F31C6 (밑에서 6번째)


➤ Verilog file

- ✓ Add file: gates.v, fa_v2.v, clb4.v, cla4.v
- ✓ New file : cla32.v, cla_clk.v, tb_cla_clk.v

32-bit CLA

➤ 32-bit CLA

 - ✓ File name : cla32.v – Module name : cla32
- ✓ 앞서 구현한 4-bit cla 8개를 instance하여 직렬로 연결하여 구현



```
module cla32(a, b, ci, s, co);  
  input [31:0] a, b;  
  input ci;  
  output [31:0] s;  
  output co;  
  
  wire c1, c2, c3, c4, c5, c6, c7;
```


Instance of cla4

```
endmodule
```

CLA with Register (1/2)


➤ cla_clk module

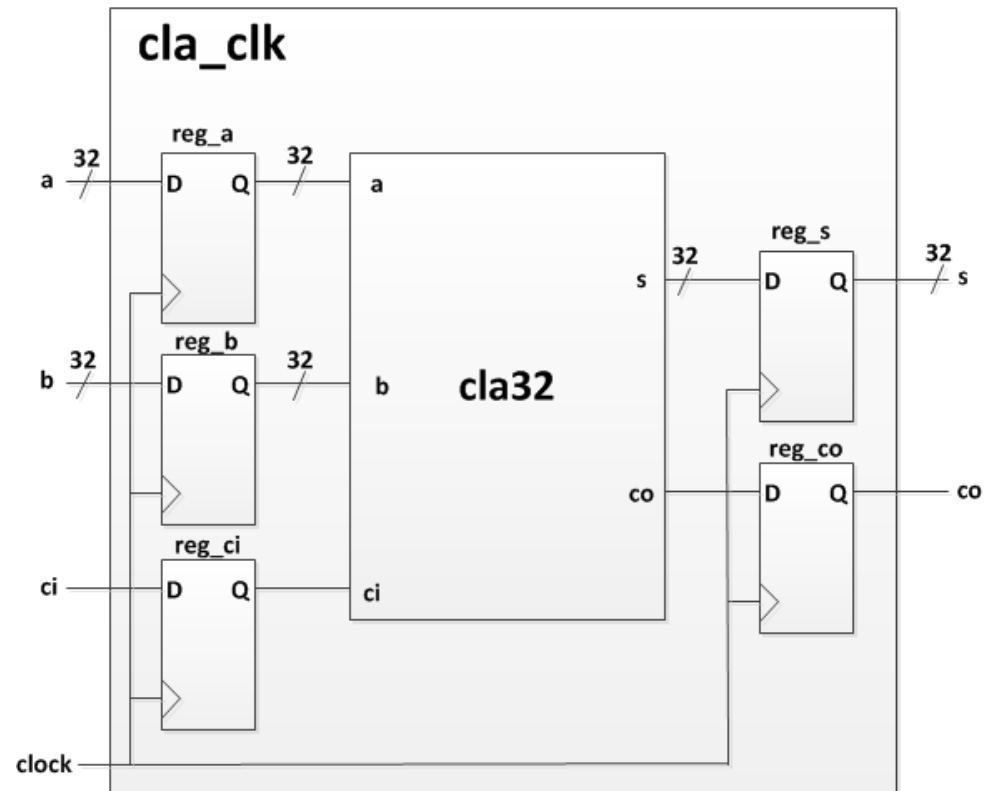- ✓ 32-bit cla에 앞 뒤로 flip-flop을 추가하여 clock과 연결하는 module
- ✓ 해당 모듈에서 clock을 인가하여 valid한 결과가 나오는 데 필요한 clock period를 확인하는 게 목적



CLA with Register (2/2)

➤ cla_clk module

 

```
module cla_clk(clk, a, b, ci, s, co);  
    input          clk;  
    input [31:0]   a, b;  
    input          ci;  
    output [31:0]   s;  
    output          co;  
  
    reg [31:0]      reg_a, reg_b;  
    reg [31:0]      reg_ci;  
    reg [31:0]      reg_s;  
    reg [31:0]      reg_co;  
  
    wire [31:0]      wire_s;  
    wire [31:0]      wire_co;  
  
    always @ (posedge clk)  
    begin  
        always  
  
        Instance of cla32  
  
        assign  
  
    end  
endmodule
```

Testbench

```
timescale 1ns/100ps

module tb_cla_clk;
    reg          clk;
    reg  [31:0]  tb_a, tb_b;
    reg          tb_ci;
    wire  [31:0] tb_s_cla;
    wire          tb_co_cla;

    parameter STEP = 10;


    cla_clk U0_cla_clk(.clk(clk), .a(tb_a), .b(tb_b), .ci(tb_ci),
        .s_cla(tb_s_cla), .co_cla(tb_co_cla));

    always #(STEP/2) clk = ~clk;


    initial
    begin

        Testbench

    end
endmodule
```

 

RTL Viewer

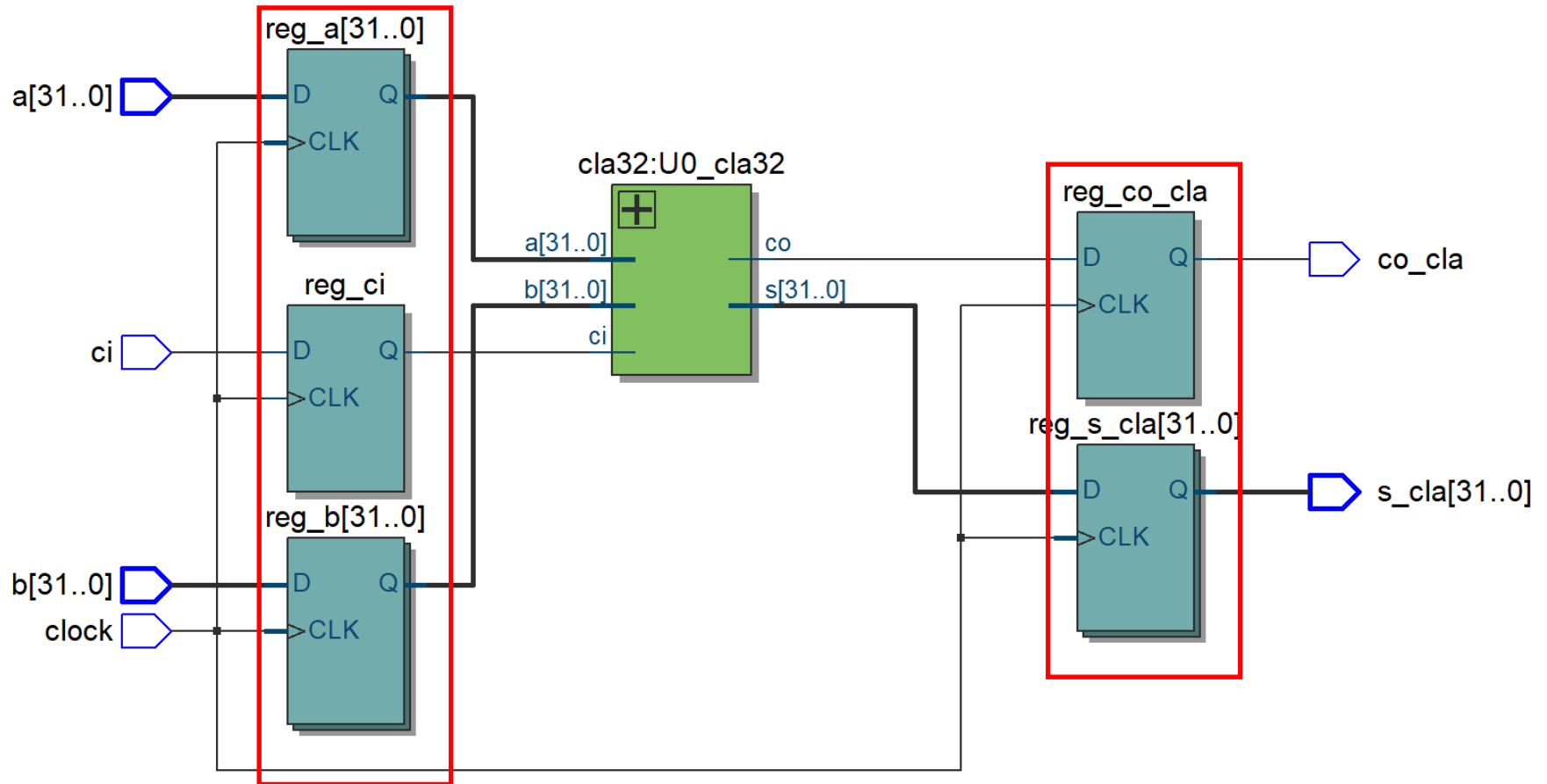



Compilation Report

➤ Flow Summary

Flow Summary	
Flow Status	Successful - [REDACTED]
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite Edition
Revision Name	[REDACTED]
Top-level Entity Name	cla_clk
Family	Cyclone V
Device	5CSXFC6D6F31C6
Timing Models	Final
Logic utilization (in ALMs)	48 / 41,910 (< 1 %)
Total registers	98
Total pins	99 / 499 (20 %)
Total virtual pins	0
Total block memory bits	0 / 5,662,720 (0 %)
Total DSP Blocks	0 / 112 (0 %)
Total HSSI RX PCSs	0 / 9 (0 %)
Total HSSI PMA RX Deserializers	0 / 9 (0 %)
Total HSSI TX PCSs	0 / 9 (0 %)
Total HSSI PMA TX Serializers	0 / 9 (0 %)
Total PLLs	0 / 15 (0 %)
Total DLLs	0 / 4 (0 %)

TimeQuest Timing Analyzer (1/2)

➤ Tools ➔ TimeQuest Timing Analyzer

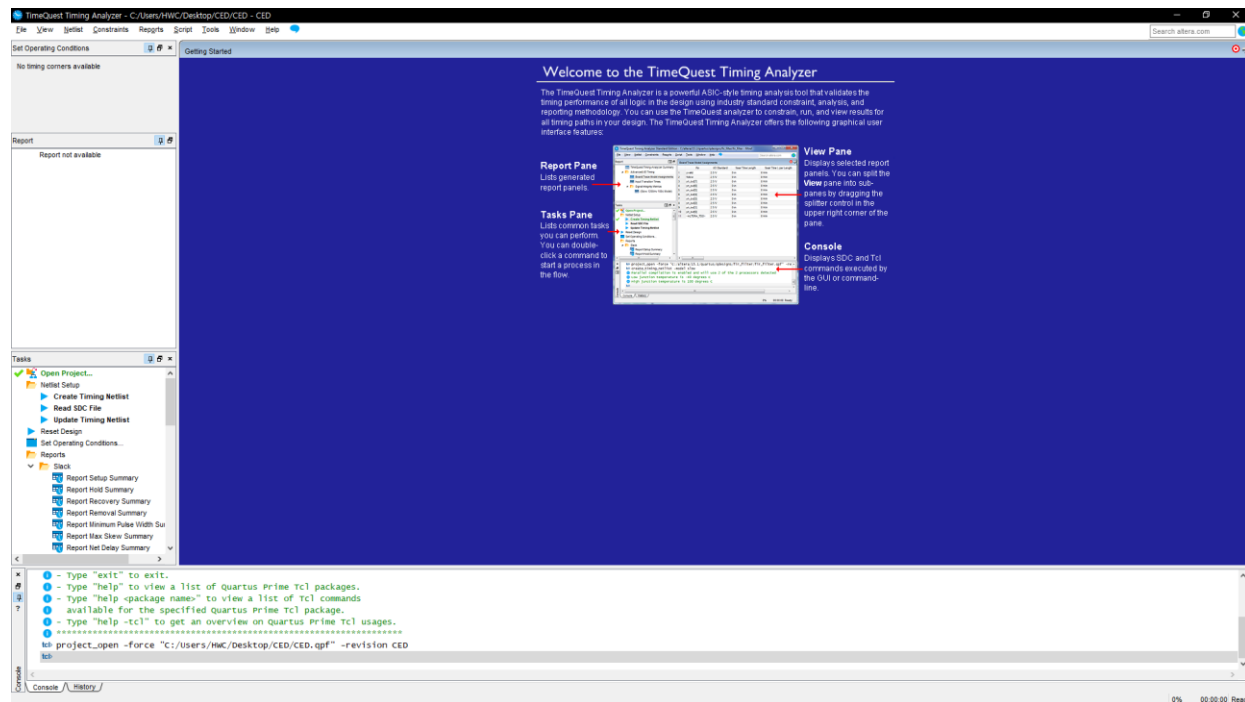 

TimeQuest Timing Analyzer (2/2)

➤ TimeQuest

✓ Report pane & Tasks Pane

✓ Report pane

- Contains any reports generated when using the tool

✓ Tasks pane

- Contains a sequence of actions that can be performed to obtain timing reports

✓ **Double click**

1. **Create Timing Netlist**



- To create a timing netlist, which will be used to perform the analysis.

2. **Read SDC File**

- To instruct the analyzer to read a Synopsys Design Constraints(SDC) file and apply the constraints to the analysis.
- Specifying the constraints enables the analyzer to determine which parts of the design will operate correctly and which will not.
- Initially, no constraints are specified and the default constraint of 1 GHz on the clock signal is applied automatically.

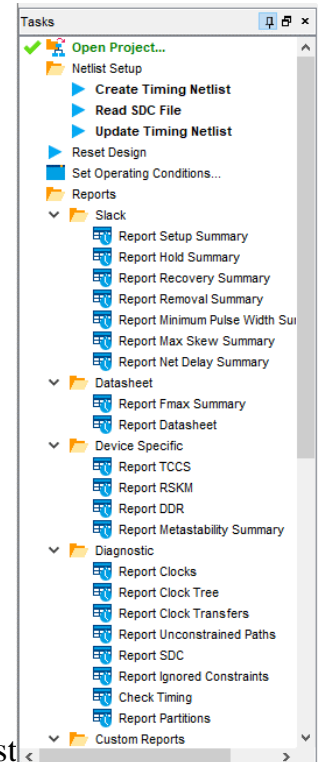 3. **Update Timing Netlist**


- To use the specified constraints to determine which parts of the circuit fail to meet them.



Timing Analysis of CLA (1/11)

- Double click
- ✓ Report Setup Summary



Slow 1100mV 85C Model			
	Clock	Slack	End Point TNS
1	clock	-3.496	-75.364

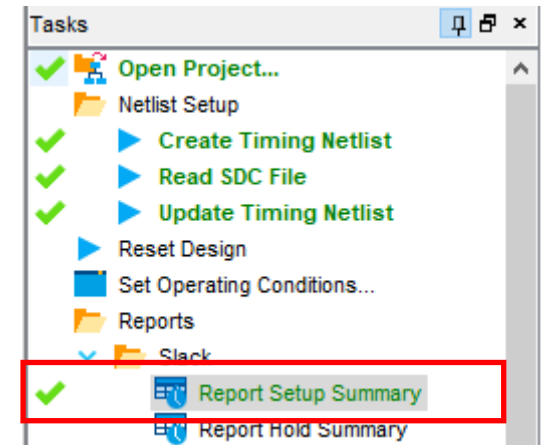

- ✓ Slack and TNS(Total Negative Slack)
 - Indicate how well the design **meets setup constraints** for each clock domain
 - Slack shows the difference between the time a signal is required to arrive at a destination FF, as per the desired clock period, and the actual arrival time.
 - **When the slack is negative, the path takes too long to compute, and the timing is considered to violate the clock constraint.**

Timing Analysis of CLA (2/11)

➤ Report Timing

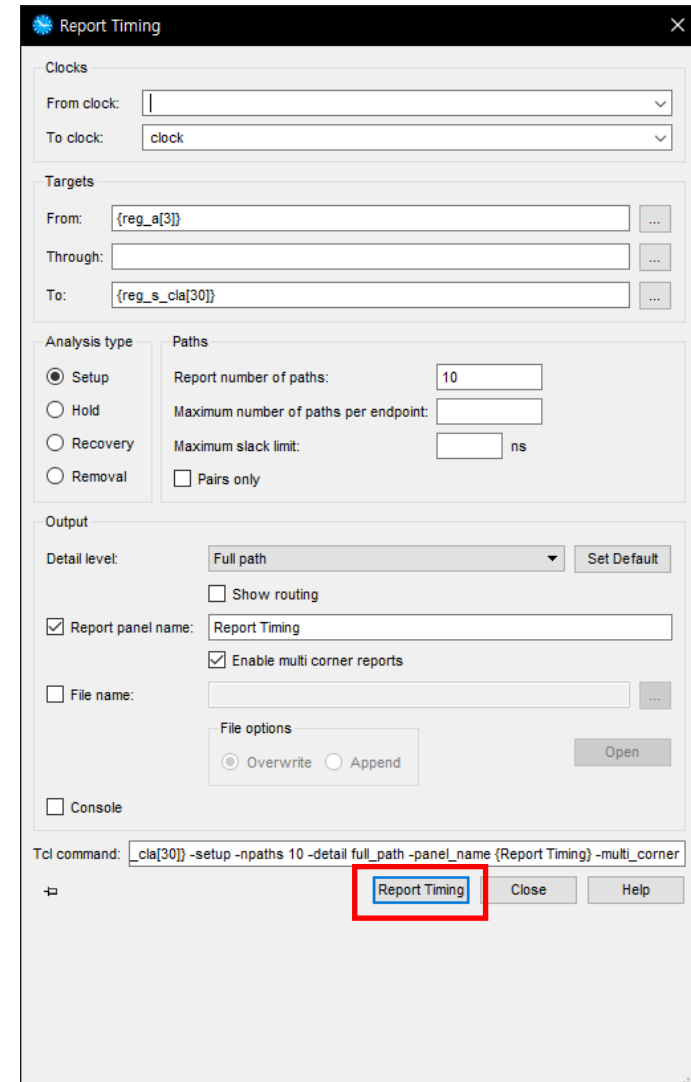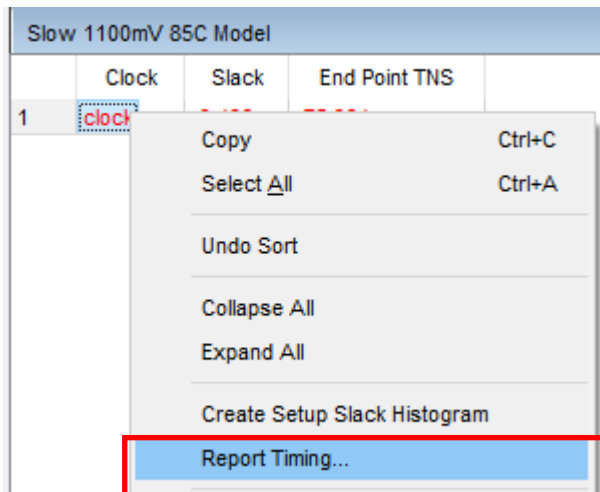

Timing Analysis of CLA (3/11)

➤ Setup: clock – Summary of Paths


Critical
Path

Slow 1100mV 85C Model								
Command Info		Summary of Paths						
	Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship	Clock Skew	Data Delay
1	-3.496	reg_a[3]	reg_s_cla[30]	clock	clock	1.000	-0.067	4.259
2	-3.486	reg_a[3]	reg_s_cla[29]	clock	clock	1.000	-0.067	4.249
3	-3.478	reg_a[3]	reg_co_cla	clock	clock	1.000	-0.067	4.241
4	-3.402	reg_a[3]	reg_s_cla[26]	clock	clock	1.000	-0.067	4.165
5	-3.327	reg_a[3]	reg_s_cla[25]	clock	clock	1.000	-0.067	4.090
6	-3.306	reg_b[2]	reg_s_cla[30]	clock	clock	1.000	-0.072	4.064
7	-3.299	reg_b[3]	reg_s_cla[30]	clock	clock	1.000	-0.072	4.057
8	-3.297	reg_b[2]	reg_s_cla[29]	clock	clock	1.000	-0.072	4.055

Timing Analysis of CLA (4/11)


➤ Setup: clock - waveform

- ✓ Slack이 음수이기 때문에 clock을 조절할 필요가 발생

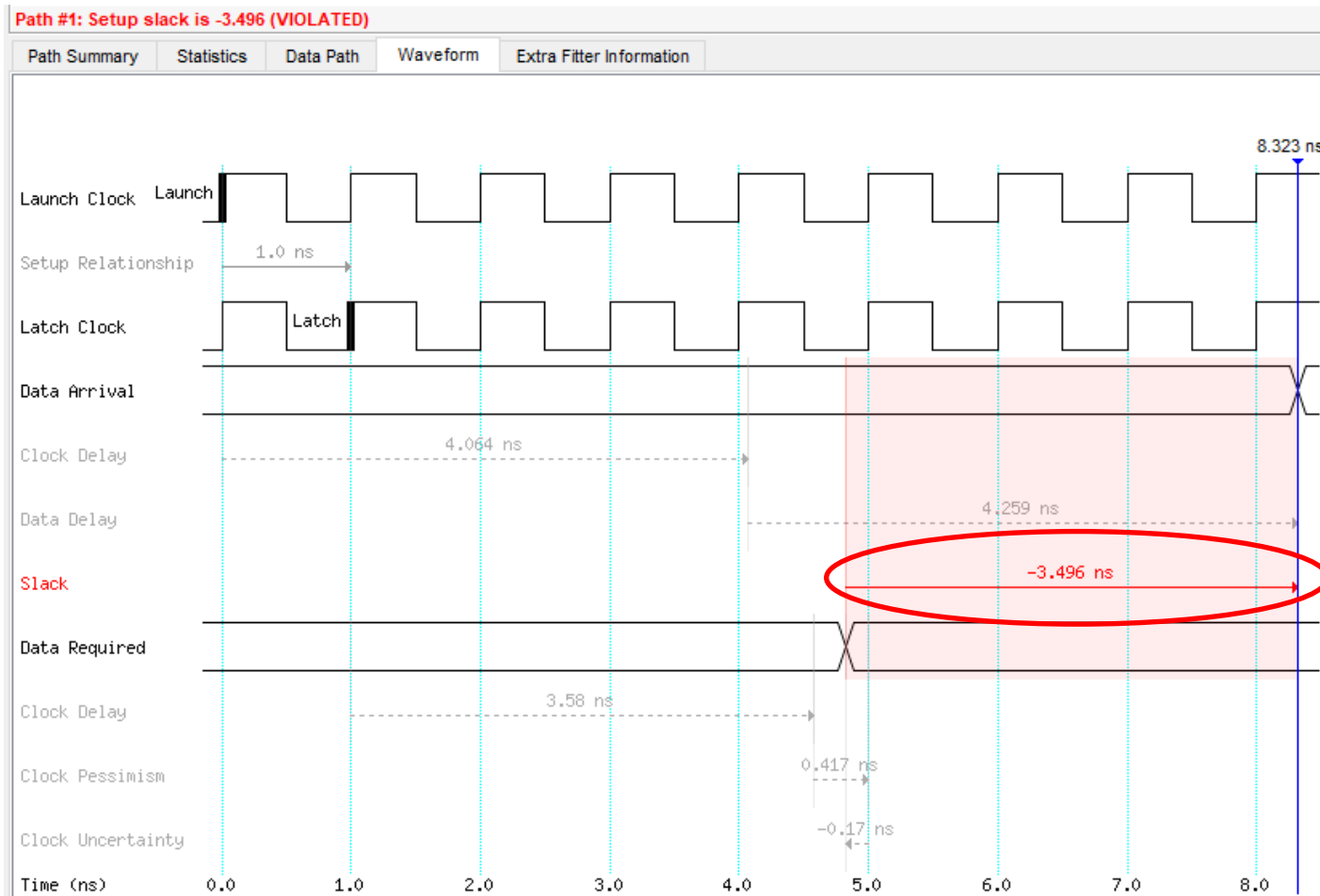


Timing Analysis of CLA (5/11)

➤ Constraints → Create Clock

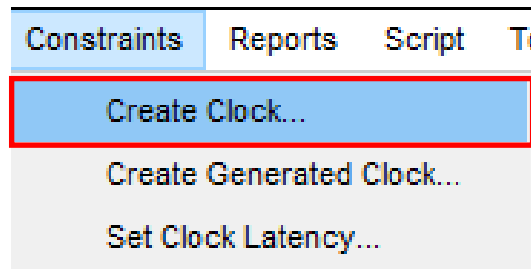



CLA module의 clock signal
name을 적을 것

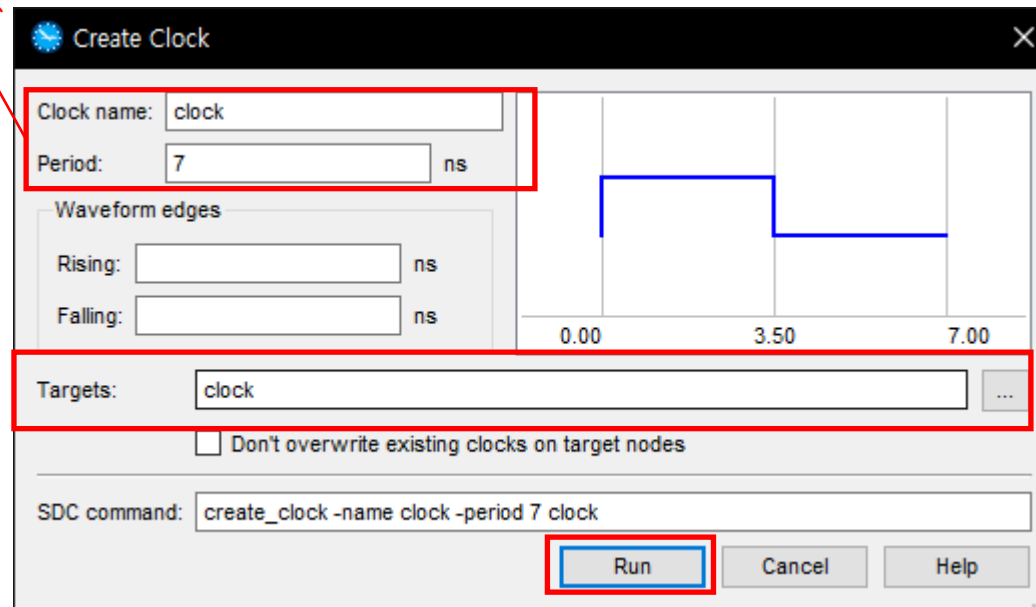

Timing Analysis of CLA (6/11)



➤ Double clock

➤ Write SDC File

 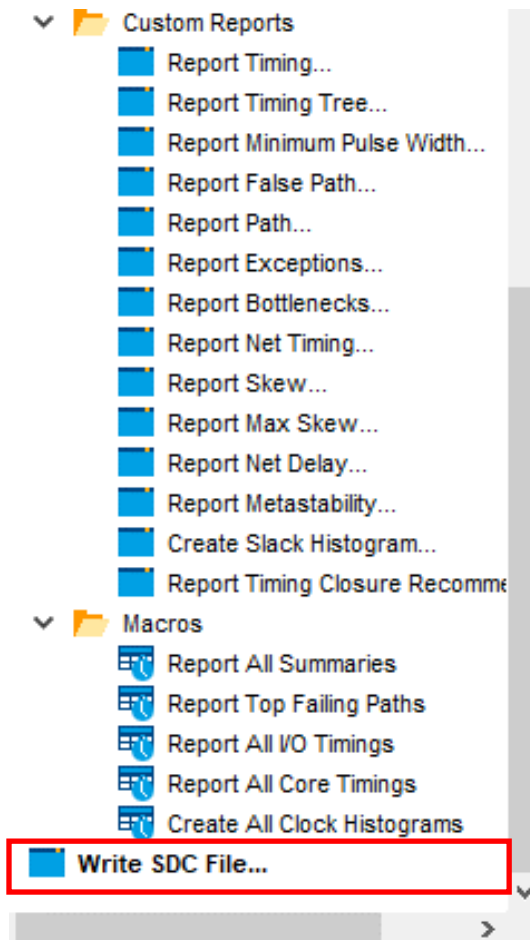


Timing Analysis of CLA (7/11)

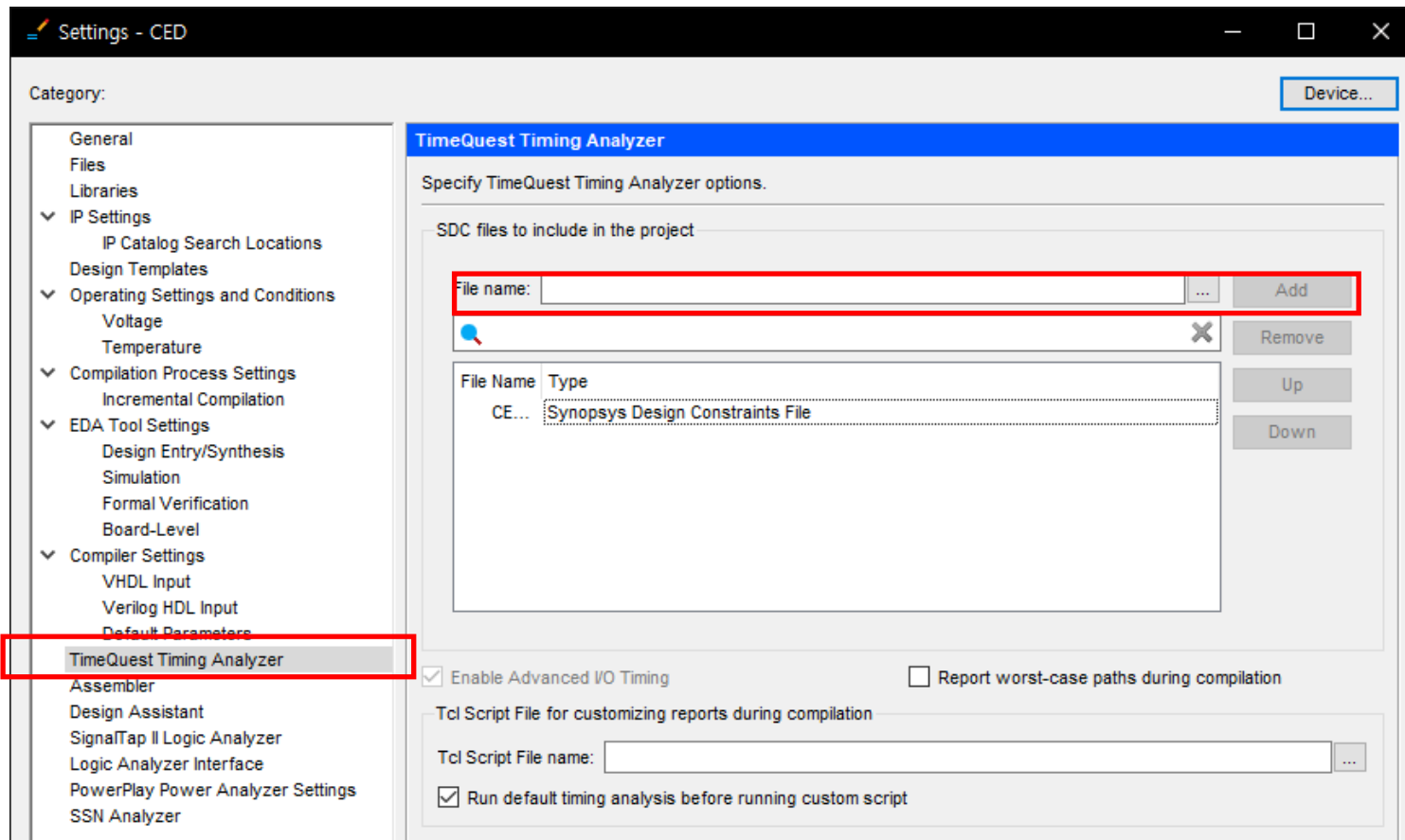 - Assignments → Settings
- TimeQuest Timing Analyzer → Add sdc file




Timing Analysis of CLA (8/11)

➤ Recompile

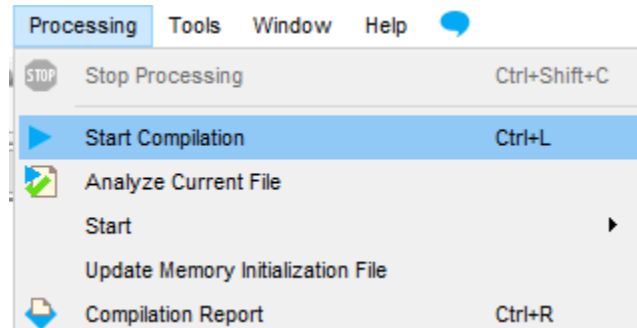

➤ Tools ➔ TimeQuest Timing Analyzer

 

Timing Analysis of CLA (9/11)

➤ Double click

- ✓ Create Timing Netlist
- ✓ Read SDC File
- ✓ Update Timing Netlist
- ✓ Report Setup Summary

Slow 1100mV 85C Model			
	Clock	Slack	End Point TNS
1	clock	0.840	0.000

Slow 1100mV 85C Model			
	Clock	Slack	End Point TNS
1	clock	0.840	0.000

Copy

Ctrl+C

Select All

Ctrl+A


Undo Sort

Collapse All

Expand All

Create Setup Slack Histogram


Report Timing...

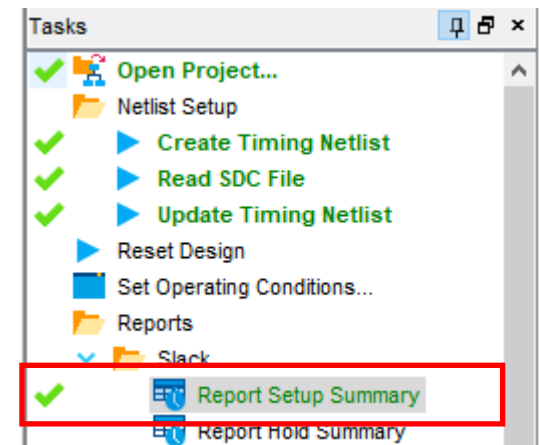

Timing Analysis of CLA (10/11)

➤ Setup: clock

 - ✓ Waveform에서 slack이 양수이기 때문에 violation이 발생하지 않음을 확인




Timing Analysis of CLA (11/11)

➤ Double click

✓ Report Fmax Summary

Slow 1100mV 85C Model				
	Fmax	Restricted Fmax	Clock Name	Note
1	162.34 MHz	162.34 MHz	clock	

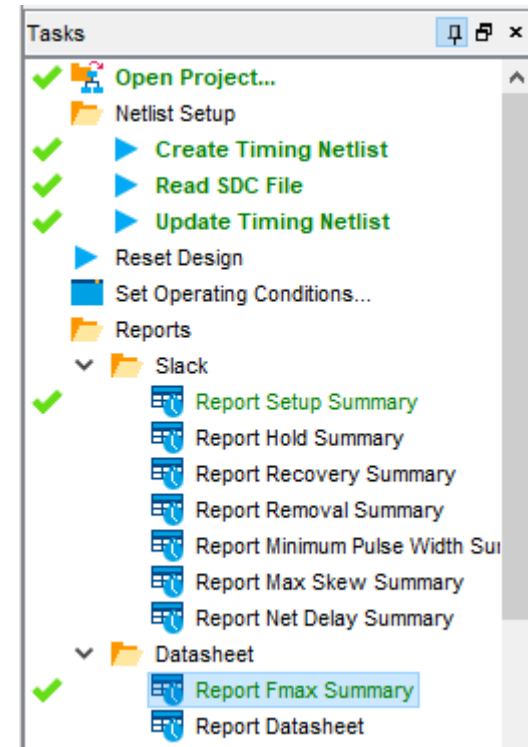- ✓ 해당 모듈(cla_clk)에서 violation이 발생하지 않는 최대의 frequency는 162.34 MHz인 것을 확인



Timing Analysis of 32-bit RCA

PRACTICE III


Timing Analysis of RCA

➤ New Project Wizard

- ✓ Project name : rca_clk
- ✓ Family & Device : Cyclone V 5CSXFC6D6F31C6 (밑에서 6번째)

➤ Verilog file

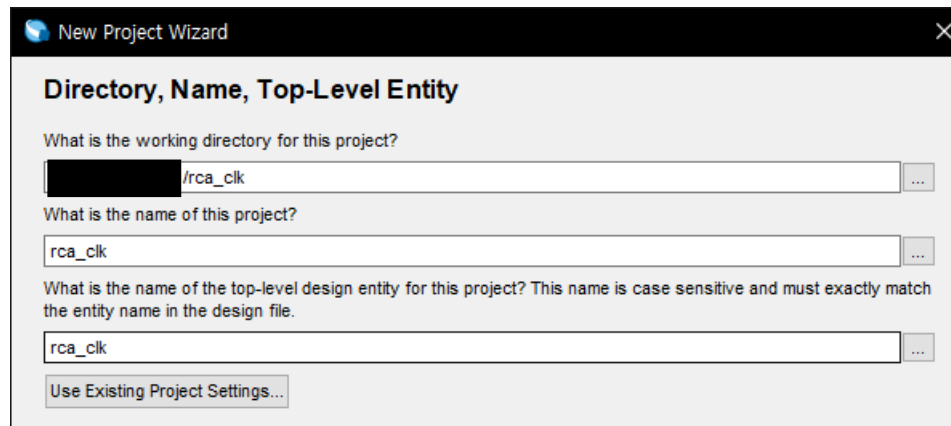- ✓ Add file: gates.v, ha.v, fa.v,
- ✓ New file : rca4.v, rca32.v, rca_clk.v



4-bits Ripple Carry Adder

➤ 4-bits RCA

```
module rca4(a, b, ci, s, co);
    input [3:0] a,b;
    input ci;
    output [3:0] s;
    output co;

    wire [2:0] c;

    fa U0_fa(.a(a[0]), .b(b[0]), .ci(ci),.s(s[0]), .co(c[0]));
    fa U1_fa(.a(a[1]), .b(b[1]), .ci(c[0]),.s(s[1]), .co(c[1]));
    fa U2_fa(.a(a[2]), .b(b[2]), .ci(c[1]),.s(s[2]), .co(c[2]));
    fa U3_fa(.a(a[3]), .b(b[3]), .ci(c[2]),.s(s[3]), .co(co));

endmodule
```

```
module fa(a,b, ci, s, co);
    input a, b, ci;
    output s, co;

    wire [2:0]w;

    ha U0_ha(.a(b), .b(ci), .s(w[0]), .co(w[1]));
    ha U1_ha(.a(a), .b(w[0]), .s(s), .co(w[2]));
    _or2 U2_or(.a(w[1]),.b(w[2]), .y(co));
endmodule
```


```
module ha(a, b, s, co);
    input a, b;
    output s, co;
    assign s = a ^ b;
    assign co = a & b;
endmodule
```

ha의 경우, 위와 같이 assign 구문을 사용하는 방법으로 변경한다.

32-bits Ripple Carry Adder

➤ 32-bits RCA

 - ✓ File name : rca32.v – Module name : rca32
- ✓ 앞서 구현한 4-bit rca 8개를 instance하여 직렬로 연결하여 구현




```
module rca32(a,b,ci,s,co);  
  input [31:0] a,b;  
  input ci;  
  output [31:0] s;  
  output co;  
  
  wire c1,c2,c3,c4,c5,c6,c7;
```

Instance of rca4

```
endmodule
```

RCA with Register

➤ rca_clk module

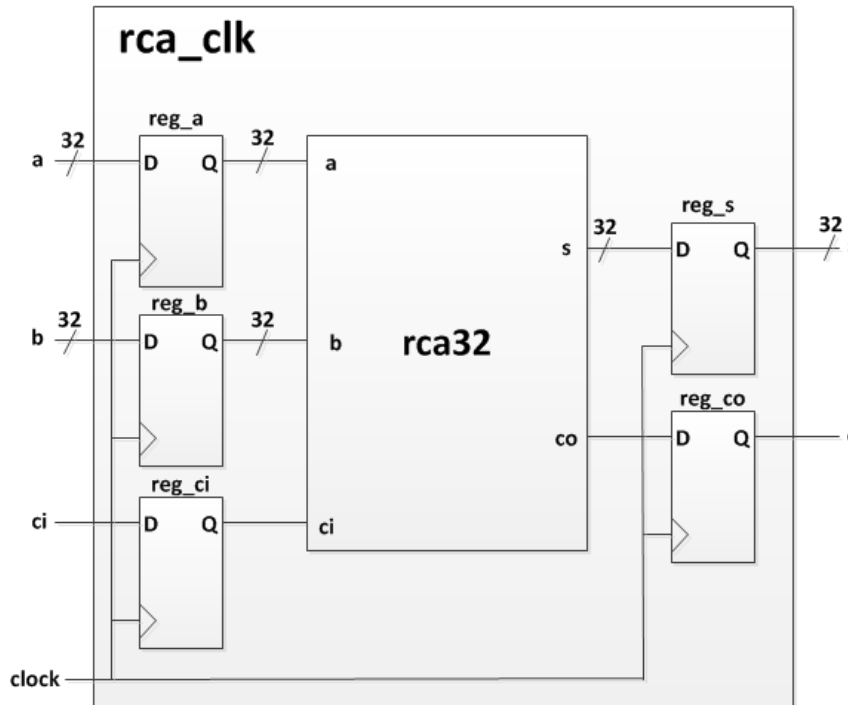

```
module rca_clk(clk,a,b,ci,s,co);  
    input          clk;  
    input [31:0]   a,b;  
    input          ci;  
    output [31:0]  s;  
    output         co;
```

```
  
    reg [31:0]     reg_a, reg_b;  
    reg            reg_ci;  
    reg [31:0]     reg_s;  
    reg            reg_co;
```

```
  
    wire [31:0]    wire_s;  
    wire           wire_co;
```

```
  
    always@(posedge clk)  
    begin
```

always

```
end
```

Instance of rca32

assign

```
endmodule
```

Testbench

```
`timescale 1ns/100ps

module tb_rca_clk;
    reg        clk;
    reg  [31:0] tb_a, tb_b;
    reg        tb_ci;
    wire  [31:0] tb_s;
    wire        tb_co;

    parameter STEP = 10;

    rca_clk U0_rca_clk(.clk(clk), .a(tb_a), .b(tb_b), .ci(tb_ci),
        .s(tb_s), .co_rca(tb_co));


    always # (STEP/2) clk = ~clk;

    initial
    begin

        Testbench

    end
endmodule
```

RTL Viewer

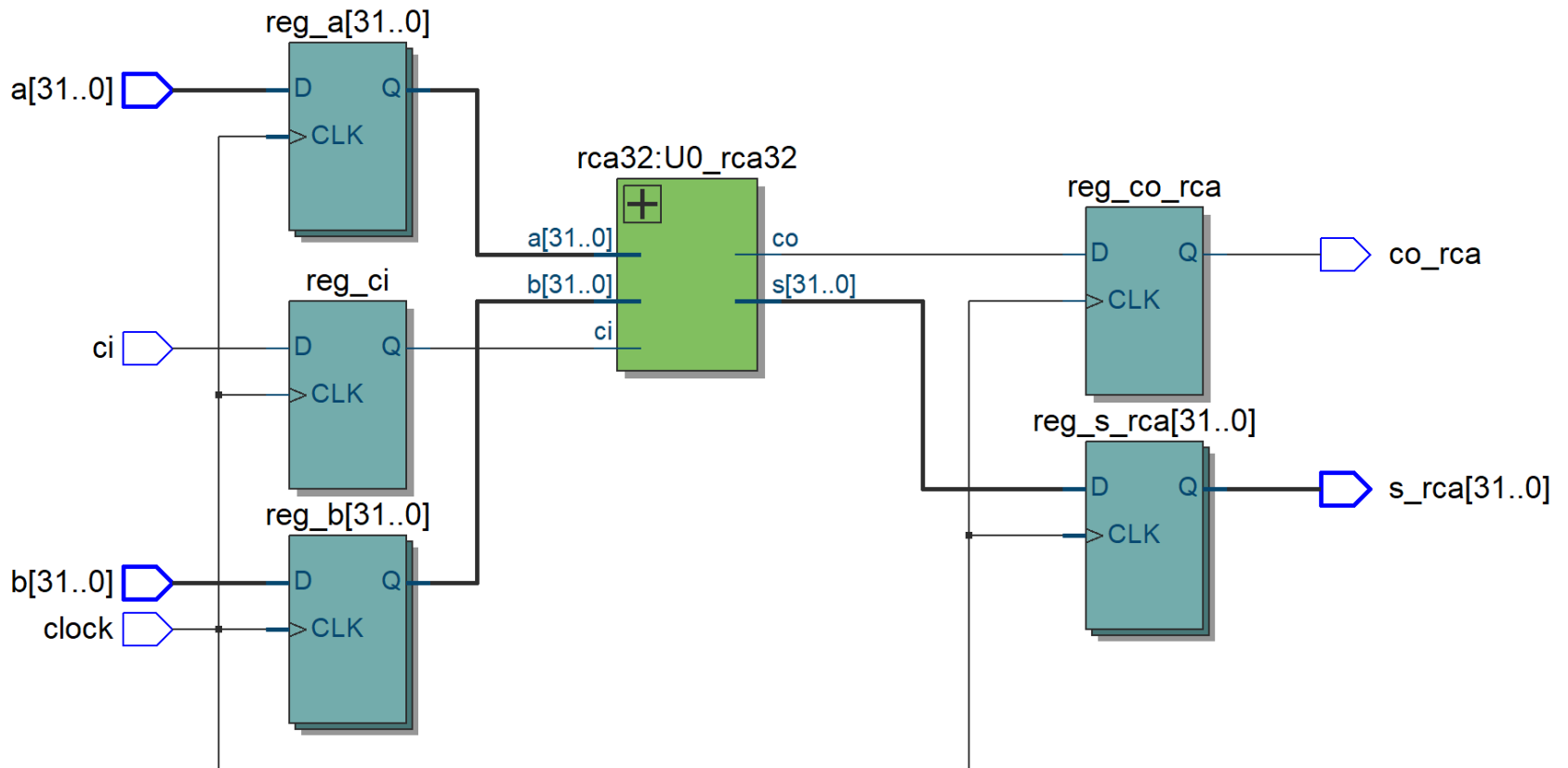

Compilation Report

➤ Flow Summary


✓ cla_clk module과 크기를 비교하여 본다.

Flow Summary	
Flow Status	Successful - [REDACTED]
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite Edition
Revision Name	[REDACTED]
Top-level Entity Name	rca_clk
Family	Cyclone V
Device	5CSXFC6D6F31C6
Timing Models	Final
Logic utilization (in ALMs)	37 / 41,910 (< 1 %)
Total registers	98
Total pins	99 / 499 (20 %)
Total virtual pins	0
Total block memory bits	0 / 5,662,720 (0 %)
Total DSP Blocks	0 / 112 (0 %)
Total HSSI RX PCSs	0 / 9 (0 %)
Total HSSI PMA RX Deserializers	0 / 9 (0 %)
Total HSSI TX PCSs	0 / 9 (0 %)
Total HSSI PMA TX Serializers	0 / 9 (0 %)
Total PLLs	0 / 15 (0 %)
Total DLLs	0 / 4 (0 %)

Timing Analysis of RCA(Cont.)

➤ TimeQuest

 - ✓ CLA에서 했던 방법처럼 TimeQuest를 사용하여 timing을 분석한다.



Slow 1100mV 85C Model				
	Fmax	Restricted Fmax	Clock Name	Note
1	?			

Assignment 3

➤ Report

- ✓ 자세한 사항은 lab document 참고

➤ Submission

- ✓ 과제 기한은 공지 참고
- ✓ 늦은 숙제는 제출 이틀 후 까지만 받음(20% 감점)

채점기준

세부사항		점수	최상	상	중	하	최하
소스코드	Source code가 잘 작성 되었는가? (Structural design으로 작성되었는가?)	10	10	8	5	3	0
	주석을 적절히 달았는가? (반드시 영어로 주석 작성)	20	20	15	10	5	0
설계검증 (보고서)	보고서를 성실히 작성하였는가? (보고서 형식에 맞추어 작성)	30	30	20	10	5	0
	합성결과를 설명하였는가?	10	10	8	5	3	0
	검증을 제대로 수행하였는가? (모든 입력 조합, waveform 설명)	30	30	20	10	5	0
총점		100					

References

- Altera Co., www.altera.com/
- 이준환, 디지털논리회로2 강의자료, 광운대학교, 컴퓨터 공학과, 2021

Q&A

THANK YOU