



# 컴퓨터공학 기초 실험2

Lab #3

Ripple Carry Adder

# **RIPPLE CARRY ADDER**

# Half Adder

- Half adder는 2개의 1-bit 입력을 받아 sum과 carry out을 출력하는 가산기

input		Output	
a	b	co	Sum s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Truth Table


a \ b	0	1
0	0	0
1	0	1

$$\text{Carry out } co = ab$$

a \ b	0	1
0	0	1
1	1	0

$$\text{Sum } s = ab' + a'b = a \oplus b$$

Karnaugh Map & Boolean Equation

 

or




Symbol

# Full Adder


- Full adder는 2개의 1-bit 입력과 1개의 1-bit carry in을 입력으로 받아 sum과 carry out을 출력하는 가산기

Input			Output	
ci	a	b	co	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Truth Table

 

Symbol

 

ci \ ab	00	01	11	10
0	0	1	0	1
1	1	0	1	0

 


ci \ ab	00	01	11	10
0	0	0	1	0
1	0	1	1	1

Boolean Equation

Karnaugh Map  
& Boolean Equation
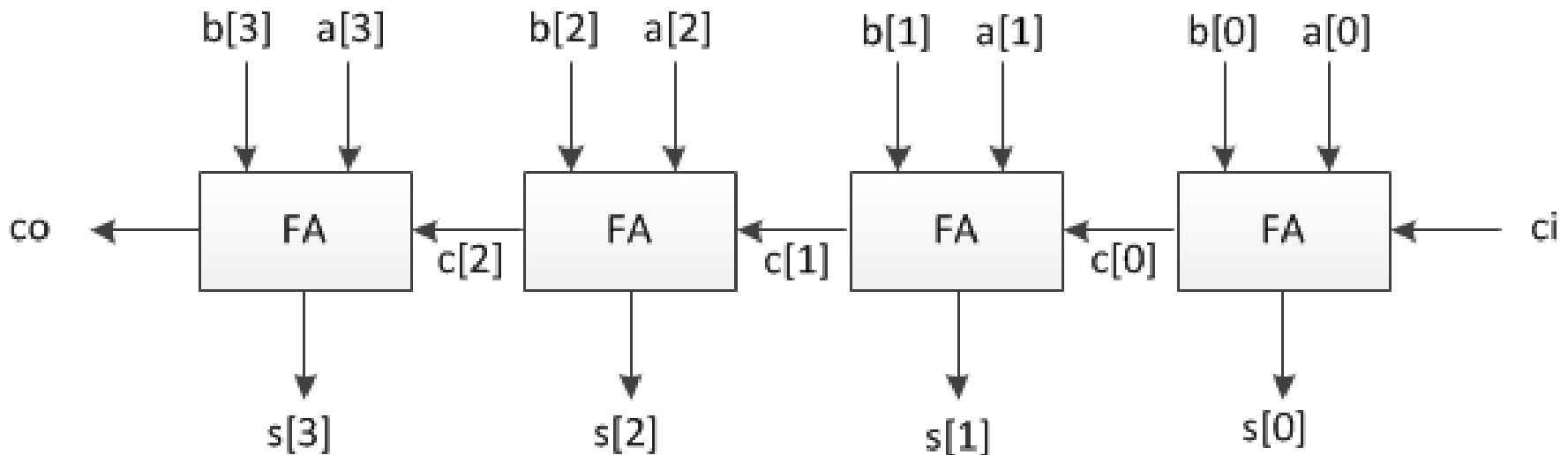
# Ripple Carry Adder

- Ripple Carry Adder는 여러 bit을 가지는 두 개의 수를 더하기 위한 간단한 형태의 가산기
  - ✓ Ripple Carry Adder는 더하고자 하는 수의 bit 개수만큼 full adder를 연결하여 구성



Half Adder & Full Adder

# **PRACTICE**

# Basic Logic Gates

## ➤ Inverter

```
module _inv(a,y);  
input a;  
output y;  
assign y=~a;  
endmodule
```

## ➤ 2-to-1 nand gate

```
module _nand2(a,b,y);  
input a,b;  
output y;  
assign y=~(a&b);  
endmodule
```

## ➤ 2-to-1 and gate

```
module _and2(a,b,y);  
input a,b;  
output y;  
assign y=a&b;  
endmodule
```

## ➤ 2-to-1 or gate

```
module _or2(a,b,y);  
input a,b;  
output y;  
assign y=a|b;  
endmodule
```

## ➤ 2-to-1 xor gate

```
module _xor2(a,b,y);  
input a, b;  
output y;  
wire inv_a, inv_b;  
wire w0, w1;
```

Instance

```
endmodule
```

## ➤ gates.v로 저장한다.

# Half Adder Project Summary

## ➤ New Project Wizard

- ✓ Project name : ha
- ✓ Family & Device : Cyclone V 5CSXFC6D6F31C6 (밑에서 6번째)

## ➤ Verilog file

- ✓ Add file : gates.v
- ✓ New file : ha.v

New Project Wizard

Directory, Name, Top-Level Entity

What is the working directory for this project?

wherever\_you\_want/ha

What is the name of this project? ~ /15.1 디렉토리에 바로 만들지 마세요

ha

What is the name of the top-level design entity for this project? This name is case sensitive and must exactly match the entity name in the design file.

ha

Use Existing Project Settings...



# Half Adder (1/3)

```
module ha(a, b, s, co);  
  input a, b;  
  output s, co ;
```

Instance

```
endmodule
```

ha.v로 저장

```
`timescale 1ns/100ps
```

```
module tb_ha;  
  reg a;  
  reg b;  
  wire s;  
  wire co;
```

Instance


```
initial  
begin
```

Testbench

tb\_ha.v로 저장



```
end  
endmodule
```

Waveform

 

# Half Adder (2/3)

## ➤ RTL Viewer

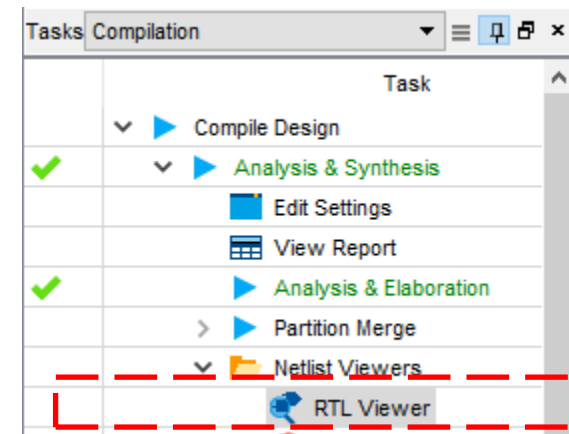 

# Half Adder (3/3)

## ➤ Flow Summary

Analysis & Synthesis Summary	
Analysis & Synthesis Status	Successful - [REDACTED]
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite Edition
Revision Name	[REDACTED]
Top-level Entity Name	ha
Family	Cyclone V
Logic utilization (in ALMs)	N/A
Total registers	0
Total pins	4
Total virtual pins	0
Total block memory bits	0
Total DSP Blocks	0
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0
Total DLLs	0

# Full Adder Project Summary

## ➤ New Project Wizard


- ✓ Project name : fa
- ✓ Family & Device : Cyclone V 5CSXFC6D6F31C6 (밑에서 6번째)

## ➤ Verilog file

- ✓ Add file : gates.v, ha.v
- ✓ New file : fa.v


# Add Files for Full Adder

- ▶ 앞서 만들었던 ha.v와 gates.v를 복사 후 추가하여 준다

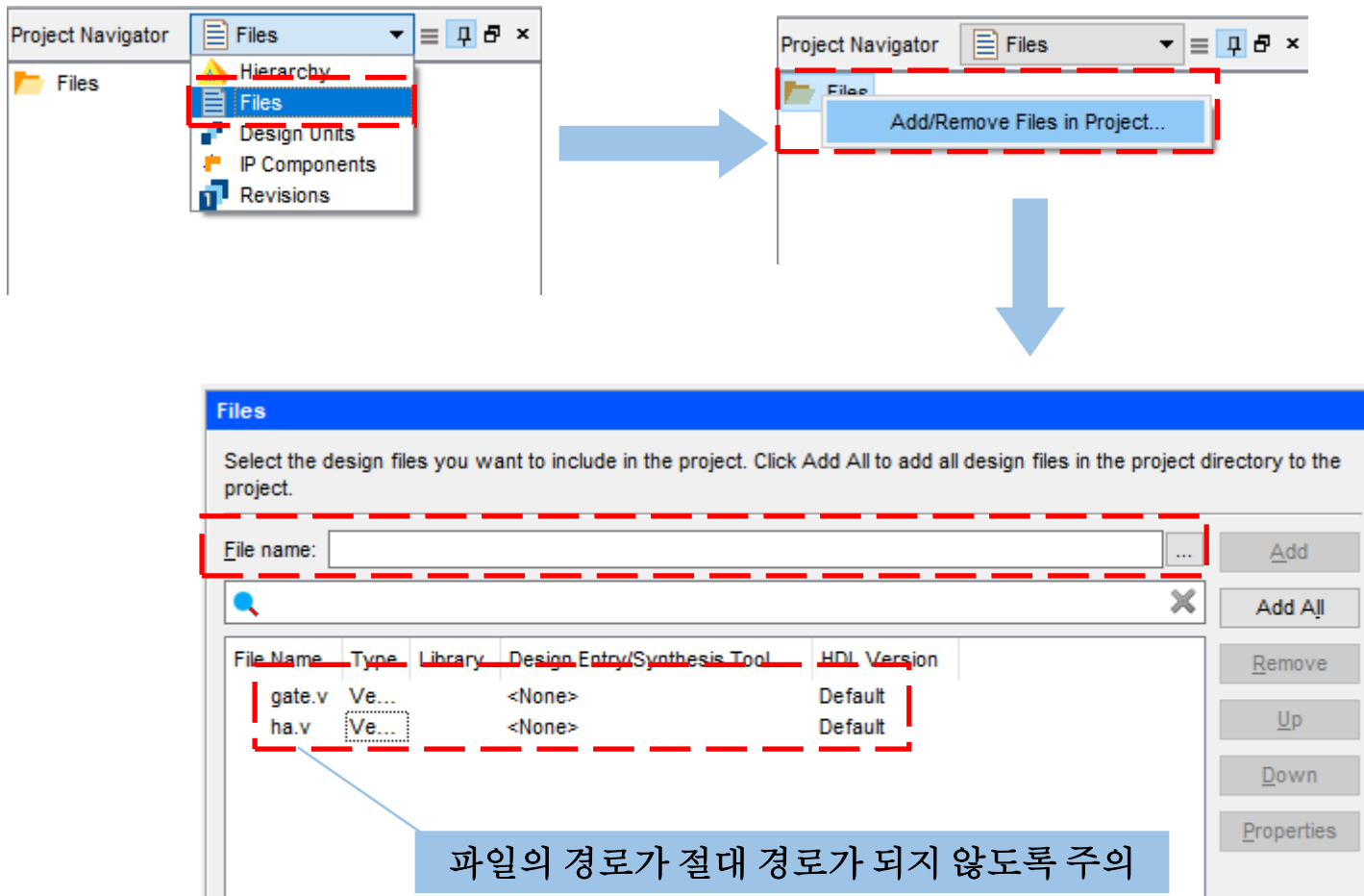

# Full Adder (1/4)

## ➤ Structural Description

 

```
module fa(a,b,ci,s,co);  
input a,b,ci;  
output s, co;  
wire c1,c2,sm;
```

Instance

```
Endmodule
```

✓ fa.v로 저장

# Full Adder (2/4)

## ➤ tb\_fa.v로 저장

```
`timescale 1ns/100ps
```

```
module tb_fa;  
  reg a, b, ci;  
  wire s, co;
```


Instance

```
  initial  
  begin
```

Testbench



```
end  
endmodule
```

## ➤ Waveform

 

# Full Adder (3/4)

## ➤ RTL Viewer

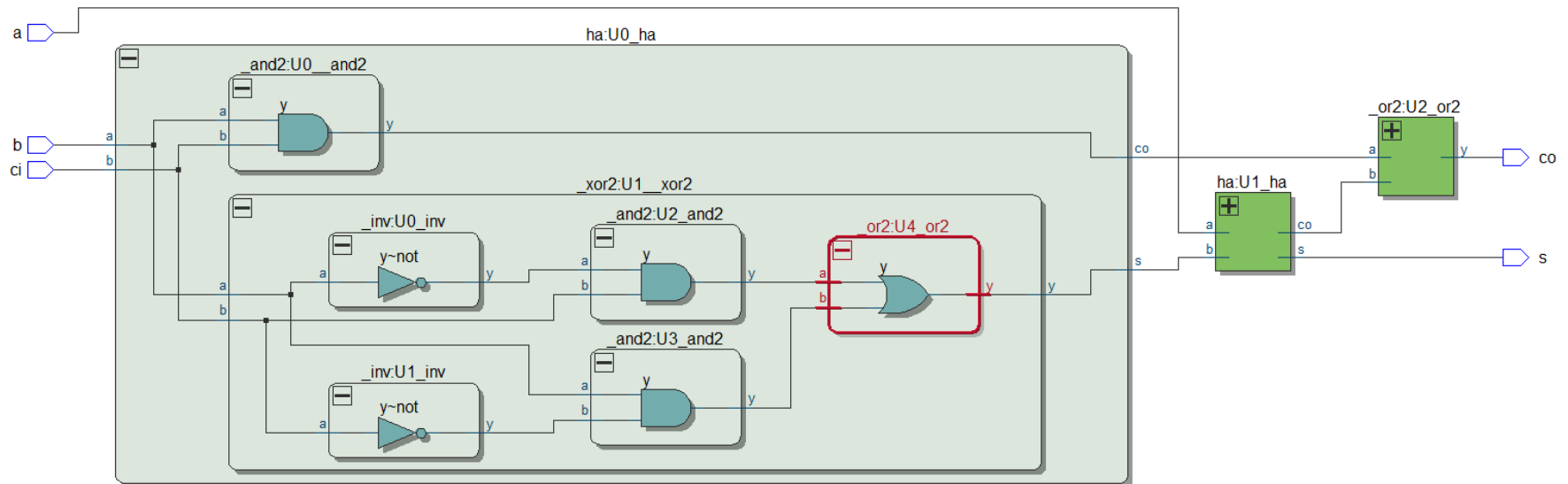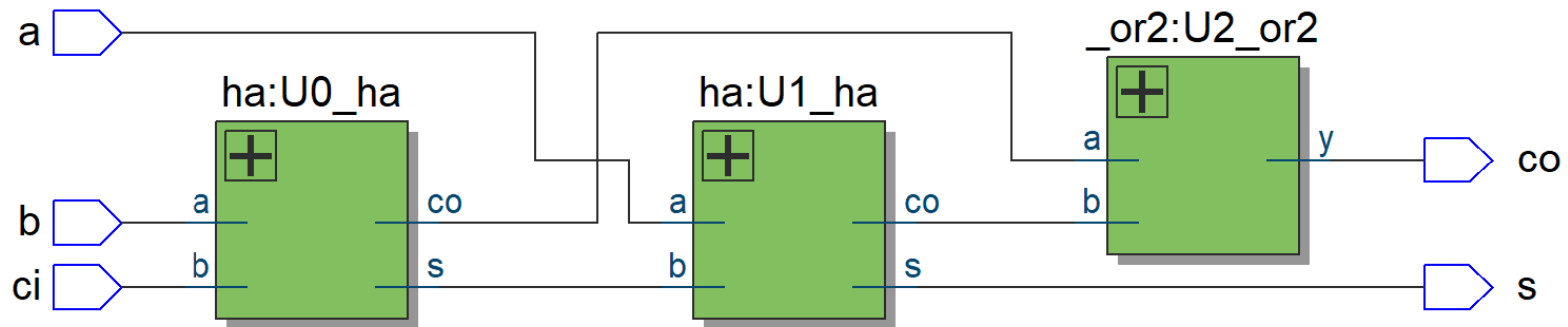



# Full Adder (4/4)

## ➤ Flow Summary

Flow Summary	
Flow Status	Successful - [REDACTED]
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite Edition
Revision Name	[REDACTED]
Top-level Entity Name	fa
Family	Cyclone V
Device	5CSXFC6D6F31C6
Timing Models	Final
Logic utilization (in ALMs)	2 / 41,910 ( < 1 % )
Total registers	0
Total pins	5 / 499 ( 1 % )
Total virtual pins	0
Total block memory bits	0 / 5,662,720 ( 0 % )
Total DSP Blocks	0 / 112 ( 0 % )
Total HSSI RX PCSs	0 / 9 ( 0 % )
Total HSSI PMA RX Deserializers	0 / 9 ( 0 % )
Total HSSI TX PCSs	0 / 9 ( 0 % )
Total HSSI PMA TX Serializers	0 / 9 ( 0 % )
Total PLLs	0 / 15 ( 0 % )
Total DLLs	0 / 4 ( 0 % )

# **RIPPLE CARRY ADDER**

# Ripple Carry Adder Project Summary

## ➤ New Project Wizard


- ✓ Project name : rca
- ✓ Family & Device : Cyclone V 5CSXFC6D6F31C6 (밑에서 6번째)

## ➤ Verilog file


- ✓ Add file : gates.v, ha.v, fa.v
- ✓ New file : rca.v

# Add Files for RCA

➤ Files에 fa.v, ha.v, gates.v를 추가

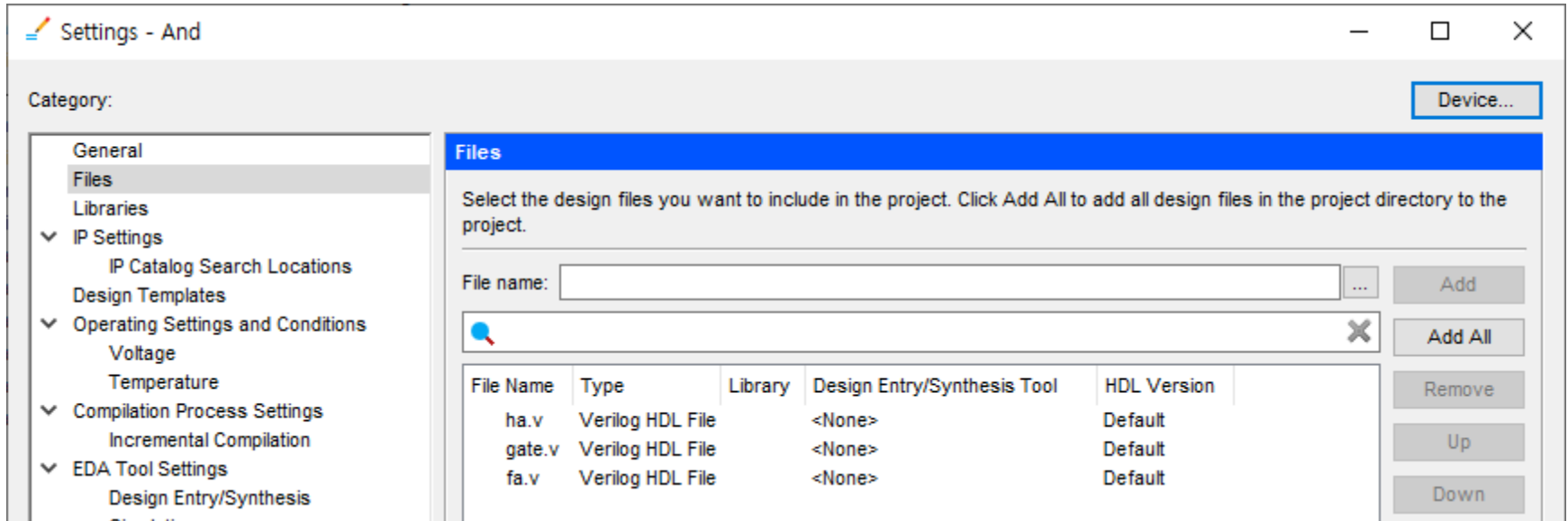

# Ripple Carry Adder (1/6)

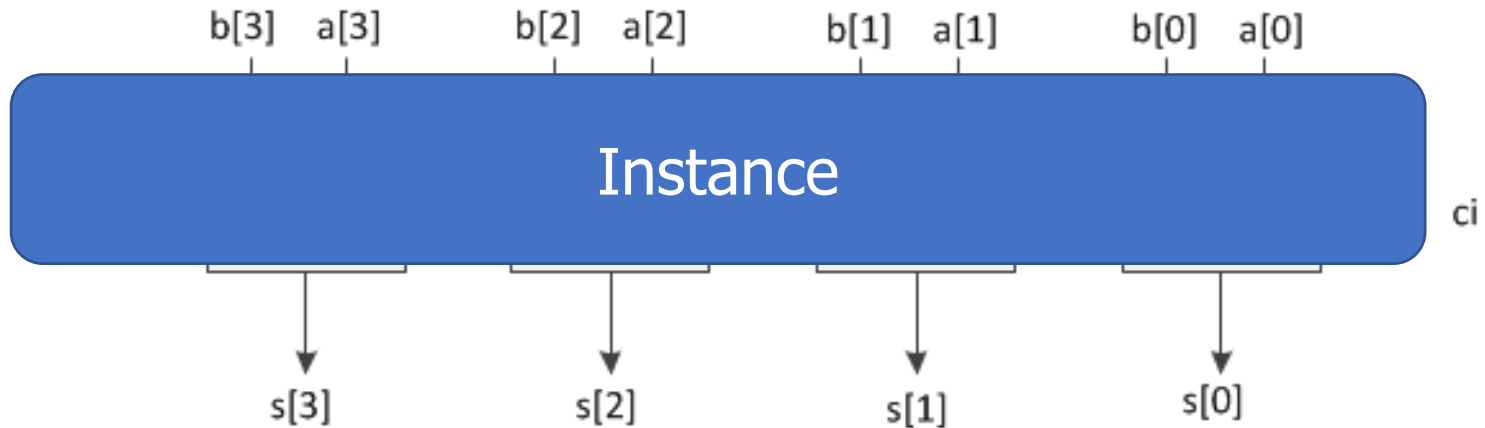

```
module rca4(a,b,ci,s,co);  
input [3:0] a,b;  
input ci;  
output [3:0] s;  
output co;  
wire [2:0] c;  
  
fa U0_fa(.a(a[0]), .b(b[0]), .ci(ci), .s(s[0]),.co(c[0]));  
fa U1_fa(.a(a[1]), .b(b[1]), .ci(c[0]),.s(s[1]), .co(c[1]));  
fa U2_fa(.a(a[2]), .b(b[2]), .ci(c[1]), .s(s[2]), .co(c[2]));  
fa U3_fa(.a(a[3]), .b(b[3]), .ci(c[2]), .s(s[3]), .co(co));  
  
endmodule
```

# Ripple Carry Adder (2/6)

## ➤ tb\_rca.v로 저장

```
`timescale 1ns/100ps

module tb_rca;
reg[3:0] tb_a, tb_b;
reg tb_ci;
wire[3:0] tb_s;
wire tb_co;
wire [4:0] tb_result;
```

Instance

```
initial
begin
```

Testbench

```
end
```

```
assign tb_result = {tb_co, tb_s};
```


```
endmodule
```

Sum과 carry out을 concatenation해서  
결과를 함께 확인


# Ripple Carry Adder (3/6)
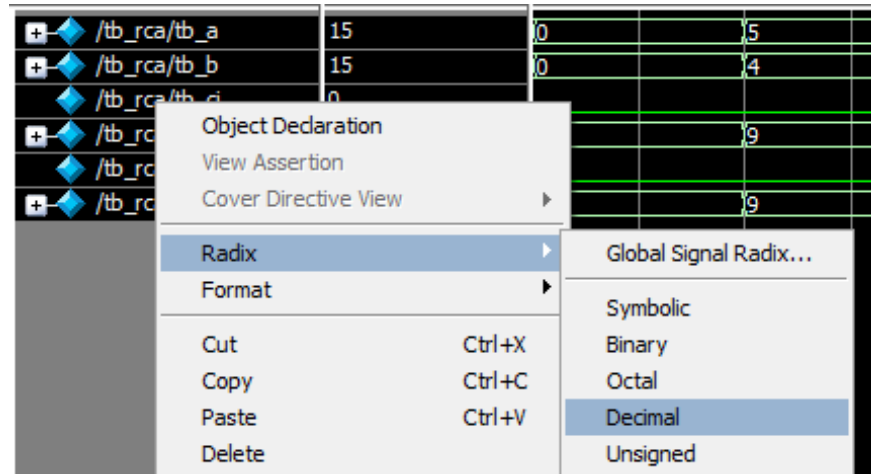
## ➤ Waveform

- ✓ 신호들을 모두 선택 → 마우스 오른쪽 클릭 → Radix → Decimal




## ➤ Decimal results

 


# Ripple Carry Adder (4/6)
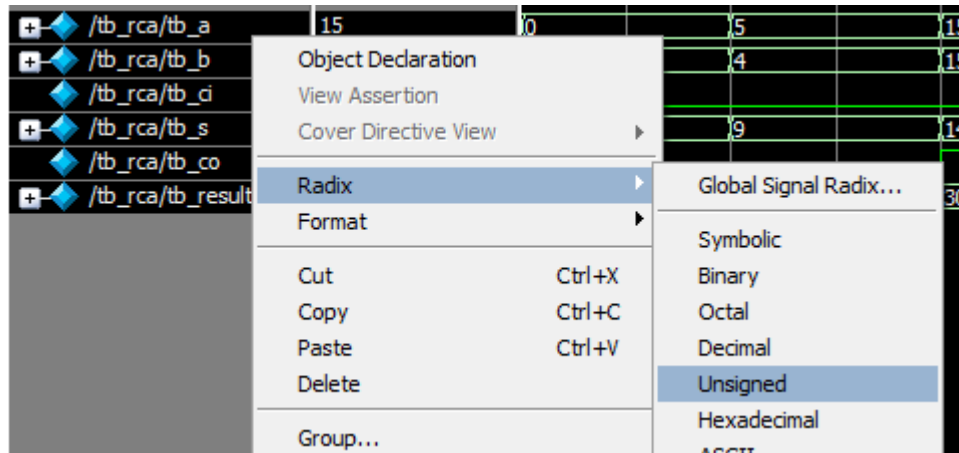
## ➤ Waveform

- ✓ 신호들을 모두 선택 → 마우스 오른쪽 클릭 → Radix → Unsigned




## ➤ Unsigned results

 



# Ripple Carry Adder (5/6)

## ➤ RTL Viewer

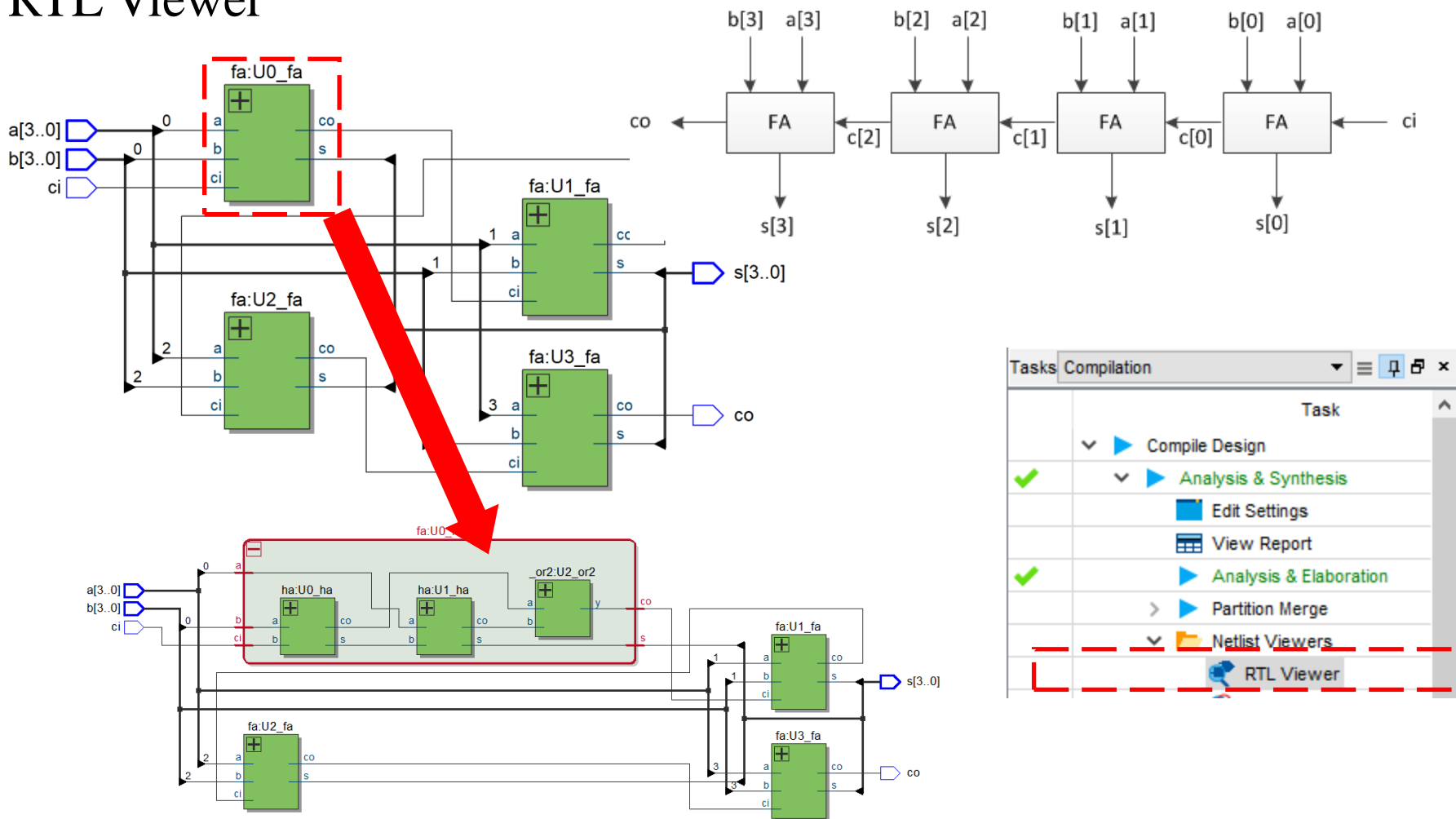

# Ripple Carry Adder (6/6)

## ➤ Flow Summary

Flow Summary	
Flow Status	Successful - [REDACTED]
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Lite Edition
Revision Name	[REDACTED]
Top-level Entity Name	rca
Family	Cyclone V
Device	5CGXFC7C7F23C8
Timing Models	Final
Logic utilization (in ALMs)	N/A until Partition Merge
Total registers	N/A until Partition Merge
Total pins	N/A until Partition Merge
Total virtual pins	N/A until Partition Merge
Total block memory bits	N/A until Partition Merge
Total PLLs	N/A until Partition Merge
Total DLLs	N/A until Partition Merge

# Assignment 2

## ➤ Report

- ✓ 자세한 사항은 Homework & Practice document 참고

## ➤ Submission

- ✓ 과제 기한은 공지 참고
- ✓ 늦은 숙제는 제출 이틀 후 까지만 받음(20% 감점)

# 채점기준

세부사항		점수	최상	상	중	하	최하
소스코드	Source code가 잘 작성 되었는가? (Structural design으로 작성되었는가?)	10	10	8	5	3	0
	주석을 적절히 달았는가? (반드시 영어로 주석 작성)	20	20	15	10	5	0
설계검증 (보고서)	보고서를 성실히 작성하였는가? (보고서 형식에 맞추어 작성)	30	30	20	10	5	0
	합성결과를 설명하였는가?	10	10	8	5	3	0
	검증을 제대로 수행하였는가? (모든 입력 조합, waveform 설명)	30	30	20	10	5	0
총점		100					

# References

- Altera Co., [www.altera.com/](http://www.altera.com/)
- 공영호, 디지털논리회로2 강의자료, 광운대학교, 컴퓨터 공학과, 2022

Q&A

**THANK YOU**